

Gate Problems on Circuit Analysis

Abstract—This problem set has questions related to RLC circuits taken from GATE papers over the last twenty years. Teachers can use the problem set for course tutorials.

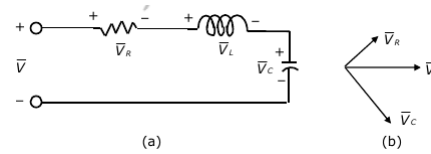


Fig. 2

- 1) In a series RLC high Q circuit, the current peaks at a frequency
 - a) Equal to the resonant frequency.
 - b) Greater than the resonant frequency.
 - c) Less than the resonant frequency.
 - d) None of the above.

- 4) For the compensated attenuator of figure 3, the impulse response under the condition $R_1 C_1 = R_2 C_2$ is:

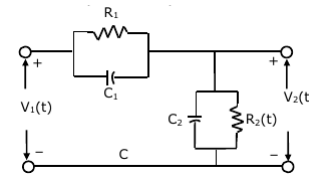


Fig. 3

- 2) The network shown in figure.1 is initially under steady state condition with the switch in position 1. The switch is moved from position 1 to position 2 at $t \neq 0$. Calculate the current $i(t)$ through R_1 after switching.

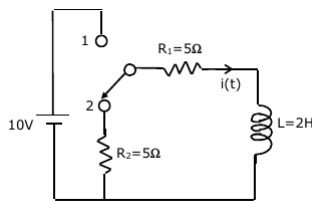


Fig. 1

- a) $\frac{R_2}{R_1 + R_2} [1 - e^{-\frac{1}{R_1 C_1}}] u(t)$

- b) $\frac{R_2}{R_1 + R_2} \delta(t)$

- c) $\frac{R_2}{R_1 + R_2} u(t)$

- d) $\frac{R_2}{R_1 + R_2} 1 - e^{-\frac{1}{R_1 C_1}} u(t)$

- 3) For the series R-L circuit of figure(a)2, the partial phasor diagram at a certain frequency is shown in figure(b). The operating frequency of the circuit is:
 - a) Equal to the resonance frequency.
 - b) Less than the resonance frequency.
 - c) Greater than resonance frequency.
 - d) Not zero.

- 5) Of the four networks N_1, N_2, N_3 and N_4 of figure 4, the networks having identical driving point functions are

- a) N_1 and N_1
- c) N_1 and N_3

- b) N_2 and N_4
- d) N_1 and N_4

- 6) In the series circuit shown in figure.5 for series

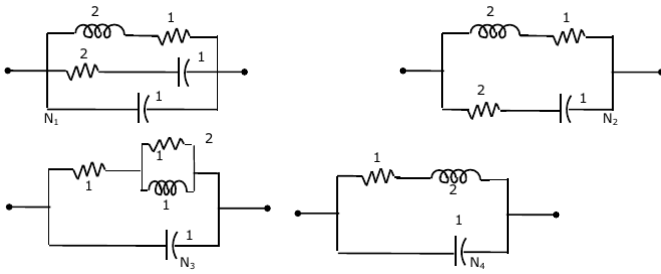


Fig. 4

resonance, the value of the coupling coefficient K will be

- a) 0.25 b) 0.5 c) 0.999 d) 1.0

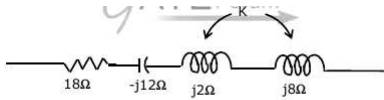


Fig. 5

7) In the circuit of figure.6, when switch S_1 is closed, the ideal ammeter M_1 reads 5A. What will be ideal voltmeter M_2 read when S_1 is kept open? (The value of E is not specified).

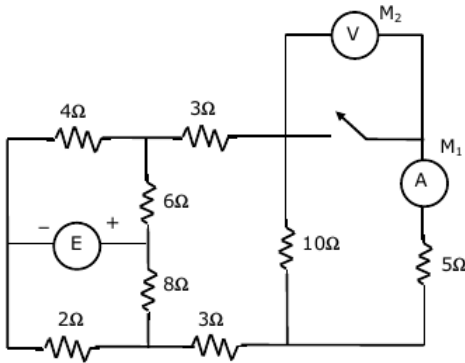


Fig. 6

8) In figure.7 A_1, A_2 and A_3 are ideal ammeters? If A_1 reads 5A, A_2 reads 12A, then A_3 should read.

- a) 7A b) 12A c) 13A d) 17A

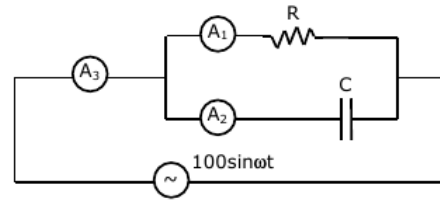


Fig. 7

9) Find the Y-parameters (short circuit admittance parameters) for the network shown in figure.8

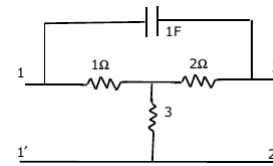


Fig. 8

10) The voltages V_{c1}, V_{c2} and V_{c3} across the capacitors in the circuit in the given figure 9, under steady state are respectively

- a) 80V, 32V, 48V c) 20V, 8V, 12V
 b) 80V, 48V, 32V d) 20V, 12V, 8V

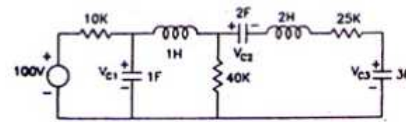


Fig. 9

11) In the circuit shown in figure 10 is (a)-(c), assuming initial voltage and currents through the inductors to be zero at the time of switching ($t=0$), then at anytime $t > 0$

a) Current increases monotonically with time

- b) Current decreases monotonically with time
- c) Current remains constant at V/R
- d) Current first increases then decreases

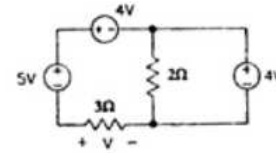


Fig. 12

- e) No current can ever flow

- a) 9V
- b) 5V
- c) 1V
- d) None of these

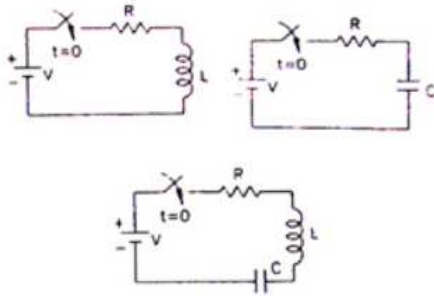


Fig. 10

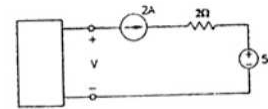


Fig. 13

12) The current i_4 in the circuit of the figure11 is equal to

15) The voltage V in the figure14 is

- a) 12A
- b) -12A
- c) 4A
- d) None of these

- a) 10V
- b) 15V
- c) 5V
- d) None of these

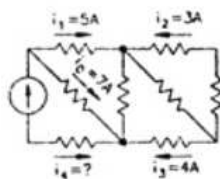


Fig. 11

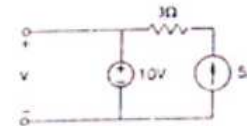


Fig. 14

13) The voltage V in the figure12 is equal to

16) In the circuit of the figure15 is the energy absorbed by the 4Ω resistor in the time interval $(0, \infty)$ is

- a) 3V
- b) -3V
- c) 5V
- d) None of these


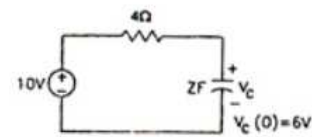


Fig. 15

14) The voltage V in the figure13 is always equal to

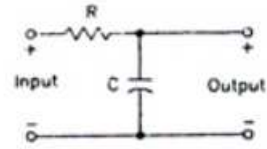- a) 36 Joules c) 256 Joules
 b) 16 Joules d) None of these



17) In the circuit of the figure16 is the equivalent impedance seen across terminals a,b is

- a) $(\frac{16}{3})\Omega$ c) $(\frac{8}{3} + 12j)\Omega$
 b) $(\frac{8}{3})\Omega$ d) None of above

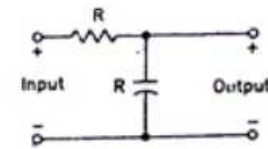
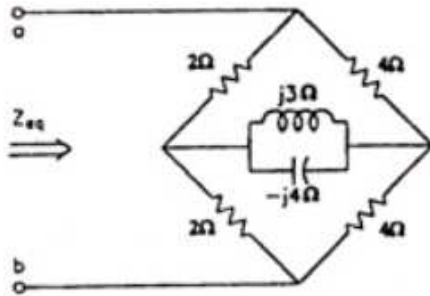


Fig. 17

Fig. 16

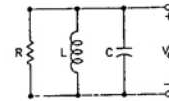


Fig. 18

18) A communication channel has first order low pass transfer function. The channel is used to transmit pulses at a symbol rate greater than the half-power frequency of the low pass function. Which of the network shown in the figure17 is can be used to equalise the received pulses?

19) In the circuit of the figure18 is $R=100\Omega$, $L=20$ nH and $C=32$ pF. The circuit is maintained at a temperature of 300k. Derive and plot the power spectral density of the voltage V_0 . Mark all the relevant points on the plot with numerical values. (The Boltzmann constant $k=1.28 \times 10^{-23}$ J/k)

20) In the circuit of figure19 when $R=0\Omega$, the current i_k equals 10A
 a) Find the value of R for which it absorbs maximum power

- b) Find the value of ε
 c) Find V_2 when $R=\infty$ (open circuit)

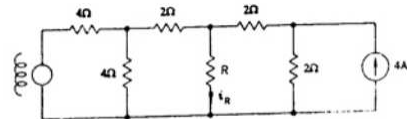


Fig. 19

21) In the circuit of the figure.20 is all currents and voltages are sinusoids of frequency ω rad/sec.

- a) Find the impedance to the right of (A,B) at $\omega=0$ rad/sec and $\omega=\infty$ rad/sec.
 b) if $\omega = \omega_0$ rad/sec and $i_1(t)=I \sin(\omega_0 t)$ A, where I is positive $\omega_0 \neq 0, \omega_0 \neq \infty$ then

find I, ω_0 and $i_2(t)$

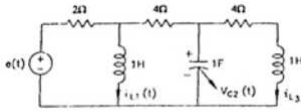


Fig. 20

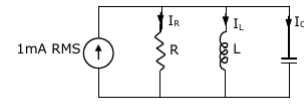


Fig. 21

- a) 0.5V b) 3.0V c) 3.5V d) 4.0V

22) The nodal method of circuit analysis is based on

a) KVL and Ohm's law

b) KCL and Ohm's law

c) KCL and KVL

d) KCL, KVL and Ohm's law

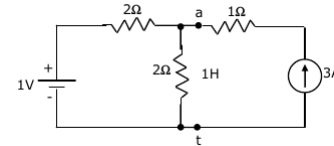


Fig. 22

23) Superposition theorem is NOT applicable to networks containing

a) Nonlinear elements

b) Dependent Voltage Sources

c) Dependent current sources

d) transformers

26) Determine the frequency of resonance and the resonant impedance of the parallel circuit shown in Figure.23. What happens when $L = CR^2$?

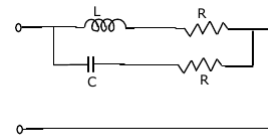


Fig. 23

24) The parallel RLC circuit shown in figure.21 is in resonance. In this circuit

a) $|I_R| < 1\text{mA}$ c) $|I_R + I_C| < 1\text{mA}$

b) $|I_R + I_L| > 1\text{mA}$ d) $|I_R + I_C| > 1\text{mA}$

27) The Thevenin equivalent voltage V_{TH} appearing between the terminals A and B of the network shown in Fig.24 is given by

a) $j16(3-j4)$ c) $16(3+j4)$

b) $j16(3+j4)$ d) $16(3-j4)$

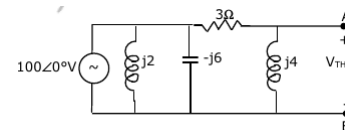


Fig. 24

25) The Voltage across the terminals a and b in figure.22 is

28) The value of R (in ohms) required for maximum power transfer in the network shown in Fig.25 is

- a) 2 b) 4 c) 8 d) 10

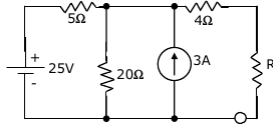


Fig. 25

29) A Delta-connected network with its Wye-equivalent is shown in Fig.26, Fig.27. The resistances R_1, R_2 and R_3 (in ohms) are respectively

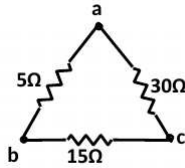


Fig. 26

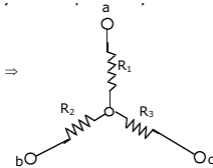


Fig. 27

30) In the circuit of Fig.28, the switch 'S' has remained open for a long time. The switch closes instantaneously at $t=0$

- a) Find V_0 for $t \leq 0$ and as $t \rightarrow \infty$
- b) Write an expression for V_0 as function of time for $0 \leq t \leq \infty$
- c) Evaluate V_0 at $t=25 \mu\text{sec}$

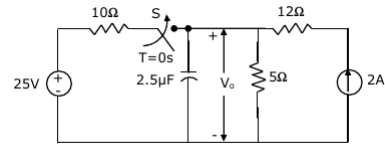


Fig. 28

31) For the network shown in Fig.29 evaluate the current I flowing through the 2Ω resistor using superposition theorem.

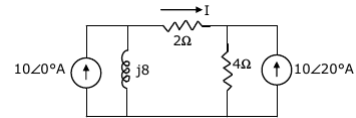


Fig. 29

32) In the circuit of Fig.30 the voltage $v(t)$ is

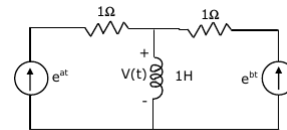


Fig. 30

- a) $e^{at} - e^{bt}$ c) $ae^{at} - be^{bt}$
- b) $e^{at} + e^{bt}$ d) $ae^{at} + be^{bt}$

33) The circuit of figure.31 represents a

- a) low pass filter c) band pass filter
- b) high pass filter d) band reject filter

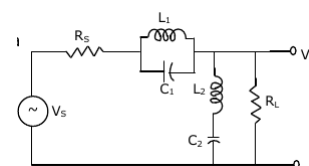


Fig. 31

34) Use the data of figure.32 .The current I in the circuit of figure(b) is

- a) -2A b) 2A c) -4A d) +4A

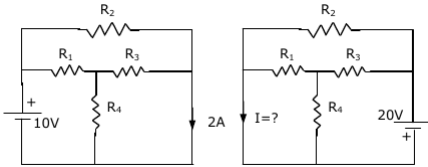


Fig. 32

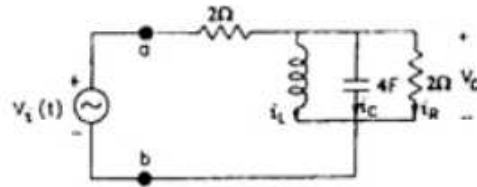


Fig. 34

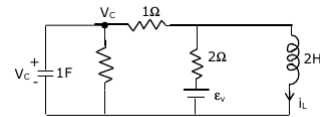


Fig. 35

35) For the circuit in figure.33

- a) Find the Thevenin equivalent of the sub circuit faced by the capacitor across the terminals a,b.

b) Find $v_c(t), t > 0$, given $V_c(0) = 0$

c) Find $i(t), t > 0$

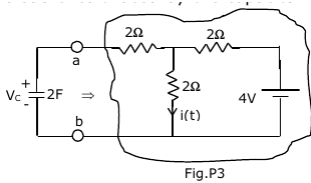


Fig. 33

38) The voltage e_0 in figure36 is

- a) 2V b) $\frac{4}{3}$ V c) 4V d) 8V

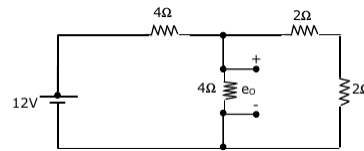


Fig. 36

39) The voltage e_0 in figure37 is

- a) 48V b) 24V c) 36V d) 28V

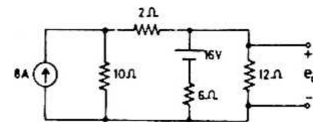


Fig. 37

36) For the circuit in figure34,which is in steady state.

- a) Find the frequency ω_0 at which the magnitude of the impedance across terminals a,b reaches a maximum.

b) Find the impedance across a,b at the frequency ω_0 .

c) if $v_s(t) = V \sin(\omega_0 t)$, find $i_L(t), i_R(t)$.

37) For the circuit in figure35,write the state equations using v_c and i_L as state variables

40) In figure38,the value of the load resistor R which maximizes the power delivered to it is

- a) 14.14Ω c) 200Ω
b) 10Ω d) 28.28Ω

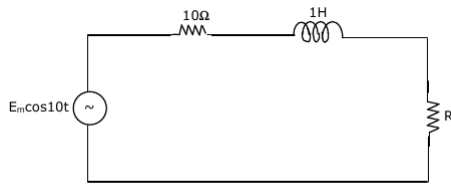


Fig. 38

- 41) When the angular frequency ω in Figure 39 is varied from 0 to ∞ , the locus of the current phasor I_2 is given by

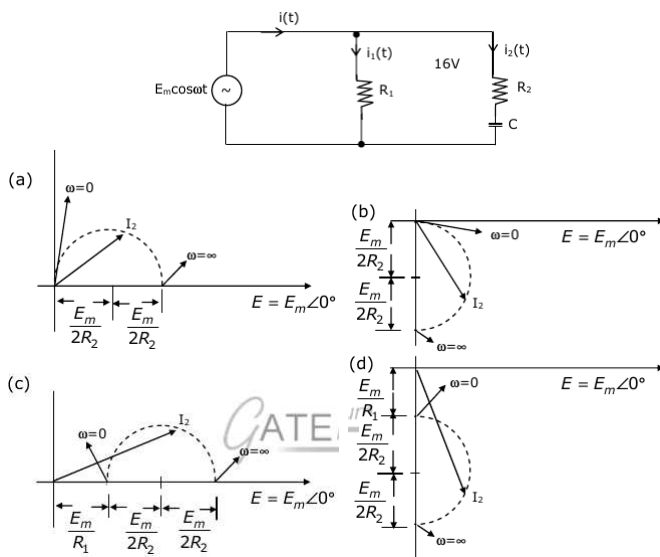


Fig. 39

- 42) For the circuit shown in figure 40, determine the phasors E_2, E_0, I and I_1

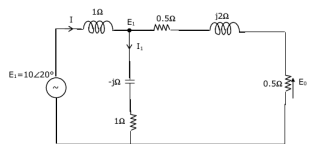


Fig. 40

- 43) The circuit shown in figure 41 is operating in steady-state with switch S_1 closed.

a) Find $i_L(0^+)$

b) Find $e_1(0^+)$

- c) Using nodal equations and Laplace transform approach, find an expression for the voltage across the capacitor for all $t > 0$.

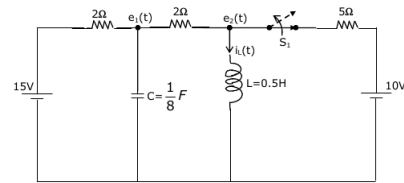


Fig. 41

- 44) The dependent current source shown in figure 42

a) delivers 80W

c) delivers 40W

b) absorbs 80W

d) absorbs 40W

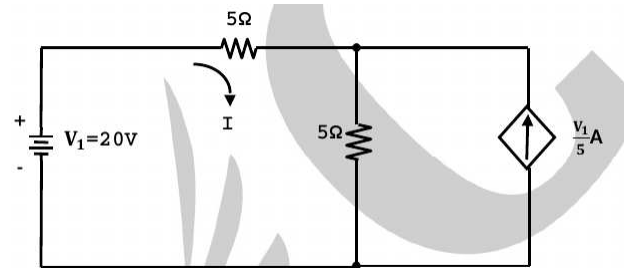


Fig. 42

- 45) In figure 43, the switch was closed for a long time before opening at $t=0$. The voltage V_x at $t=0^+$ is

a) 25V

c) -50V

b) 50V

d) 0V

- 46) In the network of figure 44, the maximum power is delivered to R_L if its value is

d) 1Ω resistance in parallel with $1F$ capacitor

51) A series RLC circuit has a resonance frequency of 1 kHz and a quality factor $Q=100$. If each R,L and C is doubled from its original value, the new Q of the circuit is

- a) 25 b) 50 c) 100 d) 200

52) The differential equation for the current $i(t)$ in the circuit of figure.48 is

- a) $2\frac{d^2i}{dt^2} + 2\frac{di}{dt} + i(t) = \sin t$
 b) $\frac{d^2i}{dt^2} + 2\frac{di}{dt} + 2i(t) = \cos t$
 c) $2\frac{d^2i}{dt^2} + 2\frac{di}{dt} + i(t) = \cos t$
 d) $\frac{d^2i}{dt^2} + 2\frac{di}{dt} + 2i(t) = \sin t$

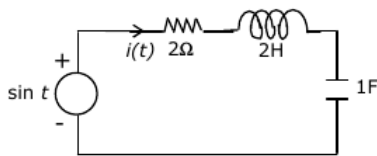


Fig. 48

53) Twelve 1Ω resistances are used as edges to form a cube. The resistance between two diagonally opposite corners of the cube is

- a) $\frac{5}{6}\Omega$ b) $\frac{1}{6}\Omega$ c) $\frac{6}{5}\Omega$ d) $\frac{3}{2}\Omega$

54) The current flowing through the resistance R in the circuit in figure.49 has the form $P \cos 4t$, where P is

- a) $(0.18+j0.72)$
 b) $(0.46+j1.90)$
 c) $-(0.18+j1.90)$

d) $-(0.192+j0.144)$

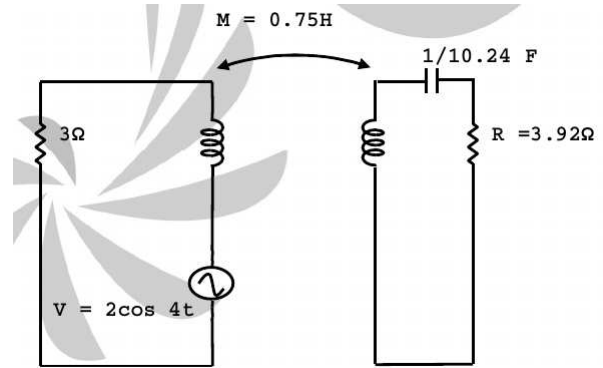


Fig. 49

55) The circuit for Q.55-56 is given in figure.50. For both the questions, assume that the switch S is in position 1 for a long time and thrown to position 2 at $t=0$. At $t=0^+$, the current i_1 is

- a) $\frac{-V}{2R}$ c) $\frac{-V}{4R}$
 b) $\frac{-V}{R}$ d) zero

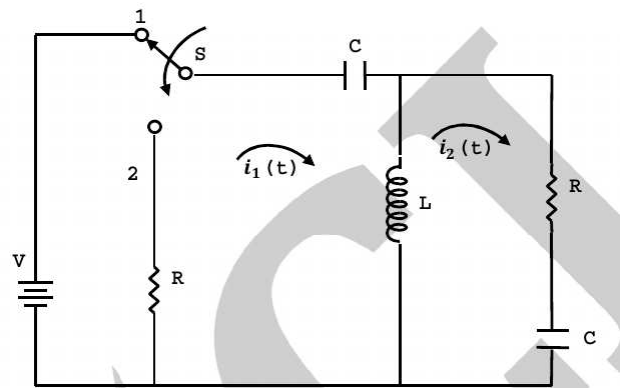


Fig. 50

56) $I_1(s)$ and $I_2(s)$ are the Laplace transforms of $i_1(t)$ and $i_2(t)$ respectively. The equations for the loop currents $I_1(s)$ and $I_2(s)$ for the circuit shown in figure Q.55-56, after the switch is brought from position 1 to position 2 at $t=0$, are

a)
$$\begin{bmatrix} R + L_s + \frac{1}{C_s} & -L_s \\ -L_s & R + \frac{1}{C_s} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{V}{s} \\ 0 \end{bmatrix}$$

$$b) \begin{bmatrix} R + L_s + \frac{1}{C_s} & -L_s \\ -L_s & R + \frac{1}{C_s} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{V}{s} \\ 0 \end{bmatrix}$$

$$c) \begin{bmatrix} R + L_s + \frac{1}{C_s} & -L_s \\ -L_s & R + L_s + \frac{1}{C_s} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{V}{s} \\ 0 \end{bmatrix}$$

$$d) \begin{bmatrix} R + L_s + \frac{1}{C_s} & -L_s \\ -L_s & R + L_s + \frac{1}{C_s} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{V}{s} \\ 0 \end{bmatrix}$$

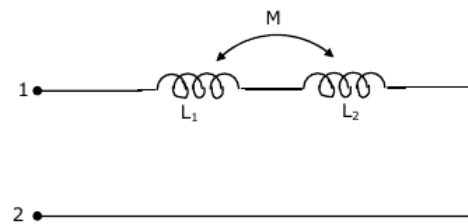


Fig. 51

a) $5\sin(2t+53.1^\circ)$ c) $25\sin(2t+53.1^\circ)$

b) $5\sin(2t-53.1^\circ)$ d) $25\sin(2t-53.1^\circ)$

57) An input voltage $v(t)=10\sqrt{2}\cos(t+10^\circ)+10\sqrt{3}\cos(2t+10^\circ)$ V is applied to a series combination of resistance $R=1\Omega$ and an inductance $L=1$ H. The resulting steady state current $i(t)$ in ampere is

a) $10\cos(t+55^\circ)+10\cos(2t+10^\circ+\tan^{-1}2)$

b) $10\cos(t+55^\circ)+10\sqrt{\frac{3}{2}}\cos(2t+55^\circ)$

c) $10\cos(t-35^\circ)+10\cos(2t+10^\circ-\tan^{-1}2)$

d) $10\cos(t-35^\circ)+10\sqrt{\frac{3}{2}}\cos(2t-35^\circ)$

58) The equivalent inductance measured between the terminals 1 and 2 for the circuit shown in figure.51, is

a) L_1+L_2+M c) L_1+L_2+2M

b) L_1+L_2-M d) L_1+L_2-2M

59) The circuit shown in figure.52 with $R=\frac{1}{3}\Omega$, $L=\frac{1}{4}$ H, $C=3$ F has input voltage $v(t)=\sin 2t$. The resulting current $i(t)$ is

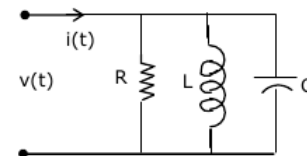


Fig. 52

60) For the circuit shown in Figure.53, the time constant $RC=1$ ms. The input voltage is $v_1(t)=\sqrt{2}\sin 10^3 t$. The output voltage $v_0(t)$ is equal to

a) $\sin(10^3 t - 45^\circ)$ c) $\sin(10^3 t - 53^\circ)$

b) $\sin(10^3 t + 45^\circ)$ d) $\sin(10^3 t + 53^\circ)$

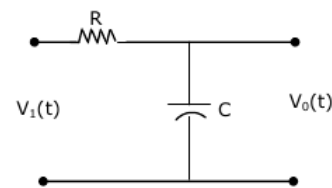


Fig. 53

61) For the R-L circuit shown in Figure.54, the input voltage $v_i(t)=u(t)$. The current $i(t)$ is

62) The circuit shown in Figure.55 has initial current $i_L(0) = 1$ A through the inductor and an

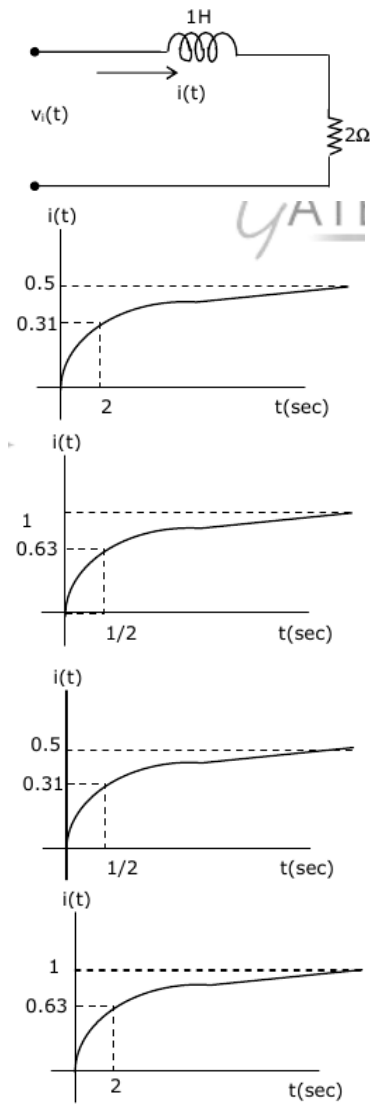


Fig. 54

initial voltage $V_c(0) = -1V$ across the capacitor. For input $v(t) = u(t)$, the Laplace transform of the current $i(t)$ for $t \geq 0$ is

- a) $\frac{s}{s^2+s+1}$ b) $\frac{s+2}{s^2+s+1}$ c) $\frac{s-2}{s^2+s+1}$ d) $\frac{s-2}{s^2+s-1}$

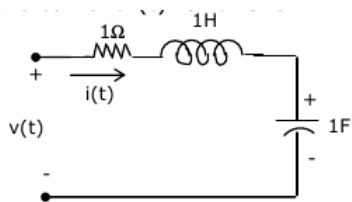


Fig. 55

63) For the circuit shown in Figure.56, the initial conditions are zero. Its transfer function $H(s) = \frac{V_c(s)}{V_i(s)}$ is

- a) $\frac{1}{s^2+10^6s+10^6}$ c) $\frac{10^3}{s^2+10^3s+10^6}$
 b) $\frac{10^6}{s^2+10^3s+10^6}$ d) $\frac{10^6}{s^2+10^6s+10^6}$

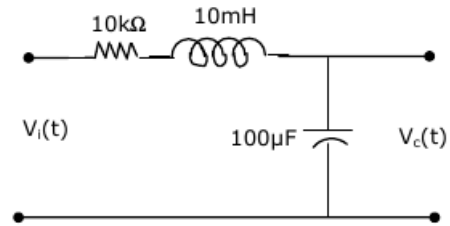


Fig. 56

64) The condition on R, L and C such that the step response $y(t)$ in figure.57 has no oscillations, is

- a) $R \geq \frac{1}{2} \sqrt{\frac{L}{C}}$ c) $R \geq 2 \sqrt{\frac{L}{C}}$
 b) $R \geq \sqrt{\frac{L}{C}}$ d) $R = \frac{1}{\sqrt{LC}}$

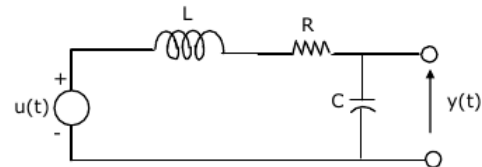


Fig. 57

65) In a series RLC circuit $R=2k\Omega$, $L=1H$ and $C=\frac{1}{400}\mu F$. The resonant frequency is

- a) 2×10^4 Hz c) 10^4 Hz
 b) $\frac{1}{\pi} \times 10^4$ Hz d) $2\pi \times 10^4$ Hz

66) The maximum power that can be transferred to the load resistor R_L from the voltage source in figure.58 is

- a) 1W b) 10W c) 0.25W d) 0.5W

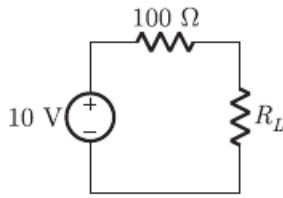


Fig. 58

- a) 5V and 2Ω c) 4V and 2Ω

- b) 7.5V and 2.5Ω d) 3V and 2.5Ω

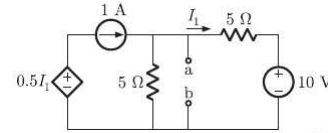


Fig. 61

67) For the circuit in figure.59 the instantaneous current $i_1(t)$ is

- a) $\frac{10\sqrt{3}}{2} \angle 90^\circ$ Amps c) $5 \angle 60^\circ$ Amps
 b) $\frac{10\sqrt{3}}{2} \angle -90^\circ$ Amps d) $5 \angle -60^\circ$ Amps

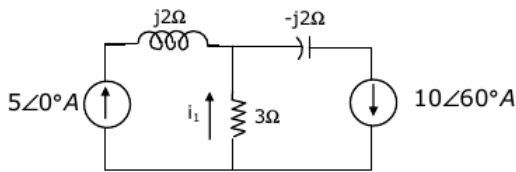


Fig. 59

70) If $R_1=R_2=R_4$ and $R_3 = 1$. 1R in the bridge circuit shown in figure.62, then the reading in the ideal voltmeter connected between a and b is

- a) 0.238 V c) -0.238 V
 b) 0.138 V d) 1 V

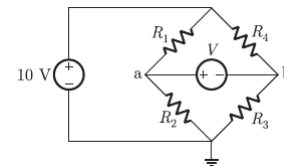


Fig. 62

68) Impedance Z as shown in figure.60 is:

- a) $j29\Omega$ c) $j19\Omega$
 b) $j9\Omega$ d) $j39\Omega$

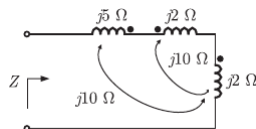


Fig. 60

71) A square pulse of 3 volts amplitude is applied to C-R circuit shown in figure.63. The capacitor is initially uncharged. The output voltage v_0 at time $t=2$ sec is

- a) 3V b) -3V c) 4V d) -4V

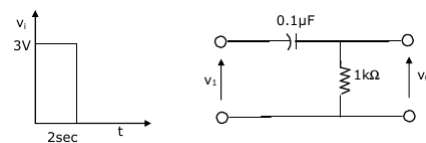


Fig. 63

69) For the circuit shown in figure.61, Thevenin's voltage and

72) In the figure.64 shown below, assume that all the capacitors are initially uncharged. If $v_i(t)=10u(t)$ Volts, $v_o(t)$ is given by

- a) $8e^{-0.004t}$ Volts c) $8u(t)$ Volts
- b) $8(1 - e^{-0.004t})$ d) 8 Volts

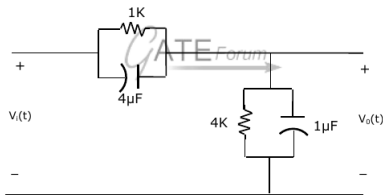


Fig. 64

73) The RC circuit shown in the figure.65 is

- a) a low-pass filter c) a band-pass filter
- b) a high-pass filter d) a band-reject filter

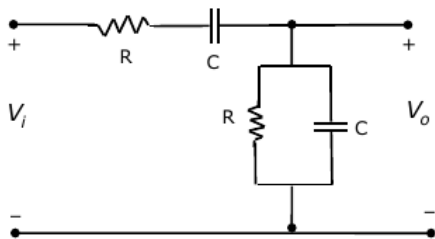


Fig. 65

74) Two series resonant filters are as shown in the figure.66. Let the 3-dB bandwidth of Filter1 be B_1 and that of Filter2 be B_2 .The value of $\frac{B_1}{B_2}$ is:

- a) 4 b) 1 c) $\frac{1}{2}$ d) $\frac{1}{4}$

75) For the circuit shown in the figure.67, the Thevenin voltage and resistance looking into X-Y

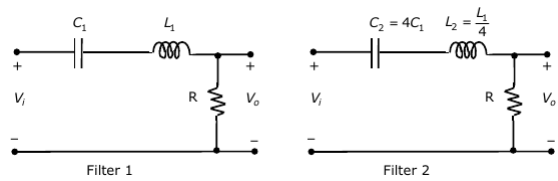


Fig. 66

- a) $\frac{4}{3}V, 2\Omega$ c) $\frac{4}{3}V, \frac{2}{3}\Omega$
- b) $4V, \frac{2}{3}\Omega$ d) $4V, 2\Omega$

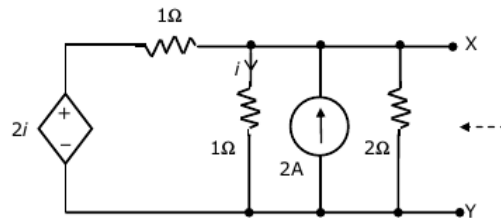


Fig. 67

76) In the circuit shown in figure.68, V_C is 0 volts at $t=0$ sec. For $t>0$, the capacitor current $i_c(t)$, where t is in seconds, is given by

- a) $0.50 \exp(-25t)$ mA c) $0.50 \exp(-12.5t)$ mA
- b) $0.25 \exp(-25t)$ mA d) $0.25 \exp(-6.25t)$ mA

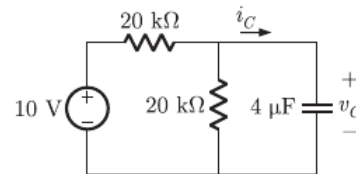


Fig. 68

77) In the AC network shown in the figure.69, the phasor voltage V_{AB} (in Volts) is:

- a) 0
- b) $5\angle 30^\circ$

c) $12.5\angle 30^\circ$

d) $17\angle 30^\circ$

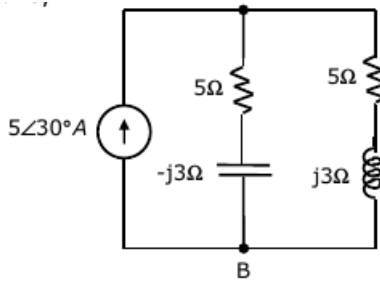


Fig. 69

78) The Thevenin's equivalent impedance Z_{TH} between the nodes P and Q in the following figure.70 is

- a) 1 b) $1+s+\frac{1}{s}$ c) $2+s+\frac{1}{s}$ d) $\frac{s^2+s+1}{s^2+2s+1}$

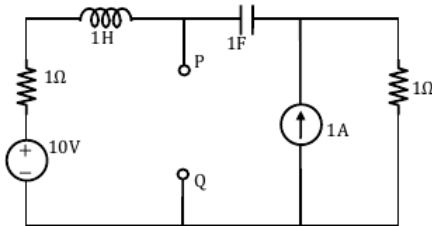


Fig. 70

79) The driving point impedance of the following figure.71 is given by $Z(s)=\frac{0.2s}{s^2+0.1s+2}$. The component values are

- a) $L=5H, R=0.5\Omega, C=0.1F$
 b) $L=0.1H, R=0.5\Omega, C=5F$
 c) $L=0.1H, R=2\Omega, C=0.1F$
 d) $L=0.1H, R=2\Omega, C=5F$

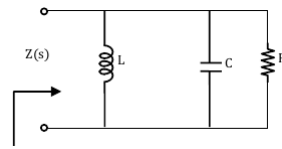


Fig. 71

current sources as indicated. The switches S1 and S2 are mechanically coupled and connected as follows

a) For $2nT \leq t < (2n+1)T$; $(n=0,1,2,..)$ S1 to P1 and S2 to P2

b) For $(2n+1)T \leq t < (2n+2)T$, $(n=0,1,2,....)$ S1 to Q1 and S2 to Q2 Assume that the capacitor has zero initial charge. Given that $u(t)$ is a unit step function, the voltage $V_c(t)$ across the capacitor is given by

- (A) $\sum_{n=0}^{\infty} (-1)^n t u(t - nT)$
 (B) $u(t) + 2 \sum_{n=1}^{\infty} (-1)^n u(t - nT)$
 (C) $tu(t) + 2 \sum_{n=1}^{\infty} (-1)^n (t - nT)u(t - nT)$
 (D) $\sum_{n=0}^{\infty} [0.5 - e^{-(t - 2nt)} + 0.5e^{-(t - 2nT - T)}]$

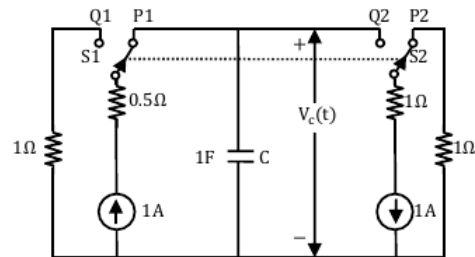


Fig. 72

81) For $t > 0$, the output voltage $V_c(t)$ is

a) $\frac{2}{\sqrt{3}}(e^{-\frac{1}{2}t} - e^{-\frac{\sqrt{3}}{2}t})$

b) $\frac{2}{\sqrt{3}}te^{-\frac{1}{2}t}$

80) The circuit shown in the figure.72 is used to charge the capacitor C alternately from two

c) $\frac{2}{\sqrt{3}}e^{-\frac{1}{2}t}\cos(\frac{\sqrt{3}}{2}t)$

d) $\frac{2}{\sqrt{3}}e^{-\frac{1}{2}t}\sin(\frac{\sqrt{3}}{2}t)$

82) For $t > 0$, the voltage across the resistor is

a) $\frac{1}{\sqrt{3}}(e^{-\frac{\sqrt{3}}{2}t} - e^{-\frac{1}{2}t})$

b) $e^{-\frac{1}{2}t}[\cos(\frac{\sqrt{3}t}{2}) - \frac{1}{\sqrt{3}}\sin(\frac{\sqrt{3}t}{2})]$

c) $\frac{2}{\sqrt{3}}e^{-\frac{1}{2}t}\sin(\frac{\sqrt{3}t}{2})$

d) $\frac{2}{\sqrt{3}}e^{-\frac{1}{2}t}\cos(\frac{\sqrt{3}t}{2})$

83) If the transfer function of the following figure.73 is $\frac{V_0(s)}{V_1(s)} = \frac{1}{2+sCR}$ the value of the load resistance R_L is

a) $\frac{R}{4}$

c) R

b) $\frac{R}{2}$

d) 2R

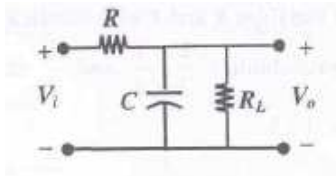


Fig. 73

84) The switch in the figure.74 shown was on position a for a long time and is moved to position b at time $t=0$. The current $i(t)$ for $t > 0$ is given by

a) $0.2e^{-125t}u(t)$ mA c) $0.2e^{-1250t}u(t)$ mA

b) $20e^{-1250t}u(t)$ mA d) $20e^{-1000t}u(t)$ mA

85) In the figure.75 shown, what value of R_L maximizes the power delivered to R_L ?

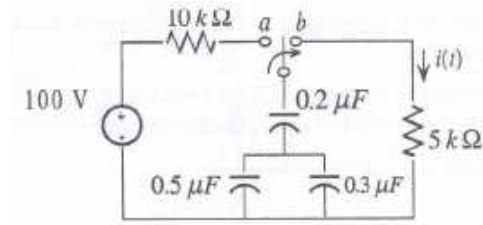


Fig. 74

a) 2.4Ω

c) 4Ω

b) $\frac{8}{3}$ Ω

d) 6Ω

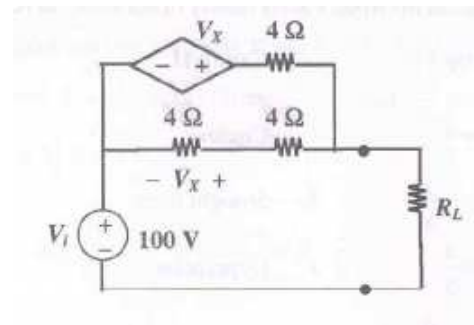


Fig. 75

86) The time domain behaviour of an RL circuit is represented by

$$L\frac{di}{dt} + Ri = V_0(1 + Be^{-\frac{Rt}{L}}\sin t)u(t).$$

For an initial current of $i(0) = \frac{V_0}{R}$, the steady state value of the current is given by

a) $i(t) \rightarrow \frac{V_0}{R}$

c) $i(t) \rightarrow \frac{V_0}{R}(1+B)$

b) $i(t) \rightarrow \frac{2V_0}{R}$

d) $i(t) \rightarrow \frac{2V_0}{R}(1+B)$

87) For parallel RLC circuit, which one of the following statements is NOT correct?

a) The bandwidth of the circuit decreases if R is increased.

b) The bandwidth of the circuit remains same if L is increased.

- c) At resonance, input impedance is a real quantity.
- d) At resonance, the magnitude of input impedance attains its minimum value.

88) In the figure.76 shown, the switch S is open for a long time and is closed at $t=0$. The current $i(t)$ for $t \geq 0^+$ is

- a) $i(t)=0.5 - 0.125e^{-1000t}$ A
- b) $i(t)=1.5 - 0.125e^{-1000t}$ A.
- c) $i(t)=0.5 - 0.5e^{-1000t}$ A
- d) $i(t)=0.375e^{-1000t}$ A

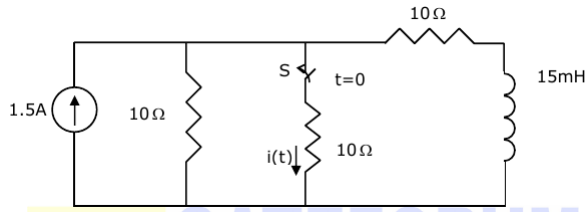


Fig. 76

89) The current I in the figure.77 shown is

- a) $-j1$ A
- b) $J1$ A
- c) 0 A
- d) 20 A

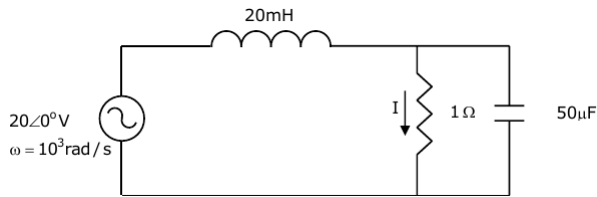


Fig. 77

90) In the figure.78 shown, the power supplied by the voltage source is

- a) 0 W
- b) 5 W

c) 10 w

d) 100 w

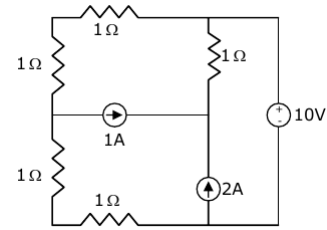


Fig. 78

91) The figure.79 shown below is driven by a sinusoidal input $V_i = V_p \cos(\frac{t}{RC})$. The steady state output V_0 is

- a) $(\frac{V_p}{3}) \cos(\frac{t}{RC})$
- b) $(\frac{V_p}{3}) \sin(\frac{t}{RC})$
- c) $(\frac{V_p}{2}) \cos(\frac{t}{RC})$
- d) $(\frac{V_p}{2}) \sin(\frac{t}{RC})$

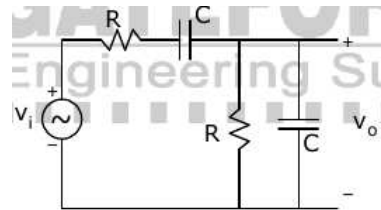


Fig. 79

92) In the figure.80 shown below, the Norton equivalent current in amperes with respect to the terminals P and Q is

- a) $6.4-j4.8$
- b) $6.56-j7.87$
- c) $10+j0$
- d) $16+j0$

93) In the figure.81 shown below, the value of R_L such that the power transferred to R_L is maximum

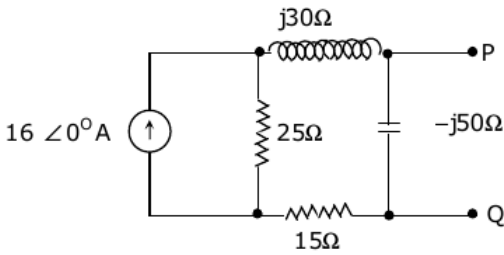


Fig. 80

- a) 5Ω
- b) 10Ω
- c) 15Ω
- d) 20Ω

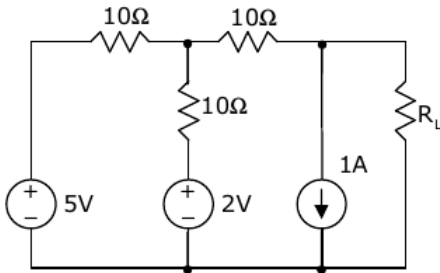


Fig. 81

- 94) In the figure.82 shown below, the current I is equal to
- a) $14\angle 0^\circ\text{A}$
 - b) $2.0\angle 0^\circ\text{A}$
 - c) $2.8\angle 0^\circ\text{A}$
 - d) $3.2\angle 0^\circ\text{A}$

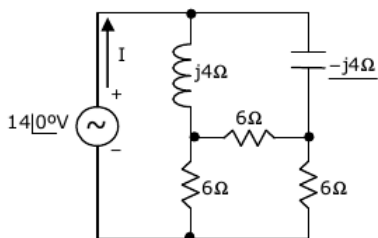


Fig. 82

- 95) In the figure.83 shown below, the initial charge on the capacitor is 2.5 mC, with the voltage

polarity as indicated. The switch is closed at time $t=0$. The current $i(t)$ at a time t after the switch is closed is

- a) $i(t)=15\exp(-2\times 10^3t)\text{A}$
- b) $i(t)=5\exp(-2\times 10^3t)\text{A}$
- c) $i(t)=10\exp(-2\times 10^3t)\text{A}$
- d) $i(t)=-5\exp(-2\times 10^3t)\text{A}$

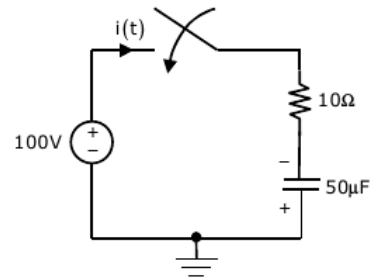


Fig. 83

96) In the figure.84 shown below, the current through the inductor is

- a) $\frac{2}{1+j}\text{A}$
- b) $\frac{-1}{1+j}\text{A}$
- c) $\frac{1}{1+j}\text{A}$
- d) 0A

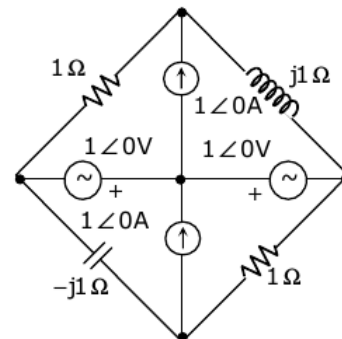


Fig. 84

97) The impedance looking into nodes 1 and 2 in the given figure.85 is

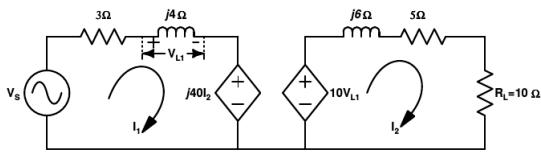


Fig. 90

R, the capacitance C, the current $i(t)$ is below:

$$V_s = R_i(t) + \frac{1}{C} \int_0^t i(t) dt.$$

Which one of the following $i(t)$ represents

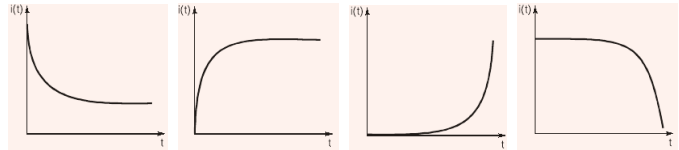


Fig. 93

103) Consider the following figure.91 for question (a) and (b).

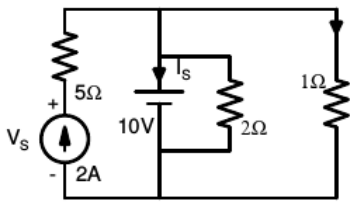


Fig. 91

106) Find the resistance R_1 from y figure.94

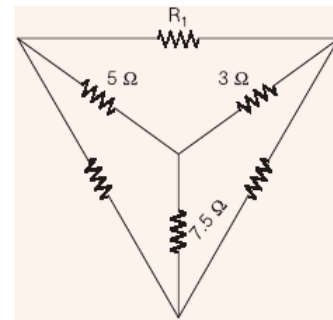


Fig. 94

a) The current I_s in Amps in the voltage source, and voltage V_s in Volts across the current source respectively, are

i) 13,-20 iii) -8,20

ii) 8,-10 iv) -13,20

b) The current in the 1Ω resistor in Amps is,

i) 2 ii) 3.33 iii) 10 iv) 12

104) Find the current I in the following Branch.,figure.92

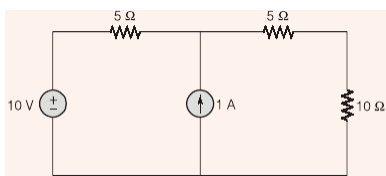


Fig. 92

107) Find the V_0 ,figure.95

a) $\frac{5}{2}V_1 - 3V_2$

b) $2V_1 - \frac{5}{2}V_2$

c) $\frac{-3}{2}V_1 - \frac{7}{2}V_2$

d) $-3V_1 + \frac{11}{2}V_2$

105) A series R_c figure.93 is connected to DC voltage source at time $t_0=0$.The relation between the source voltage V_s ,the resistance

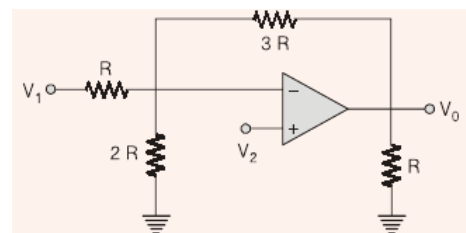


Fig. 95

108) For the figure.96 given below, what will be the largest value of arm when it is converted into delta form.

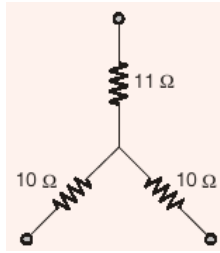


Fig. 96

109) For the given figure.97, the value of capacitor is in mF. So that the system will be critically damped is

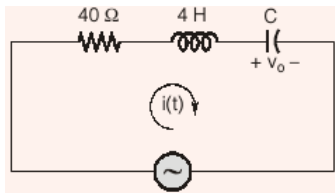


Fig. 97

110) Where $R=1\Omega, i_1 = 2A, i_4 = -1A, i_5 = -4A$. Then which of the following is correct, figure.98

- a) $i_6=5A$
- b) $i_3=-4A$
- c) Given data sufficient to tell these currents are not possible
- d) Data is not sufficient to find i_2, i_3, i_6

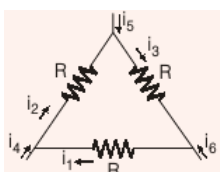


Fig. 98

111) In the figure.99 shown, at resonance, the amplitude of the sinusoidal voltage (in Volts) across the capacitor is

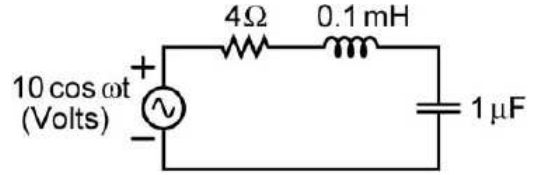


Fig. 99

112) In the network shown in the figure.100, all resistors are identical with $R=300\Omega$. The resistance R_{ab} (in Ω) of the network is

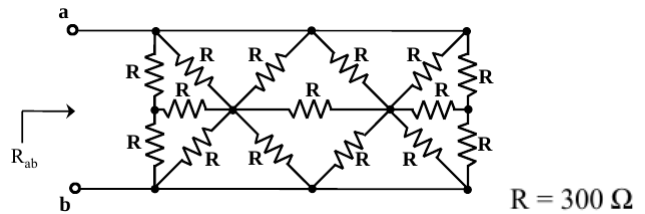


Fig. 100

113) In the given figure.101, the values of V_1 and V_2 respectively are

- a) 5V, 25V
- b) 10V, 30V
- c) 15V, 35V
- d) 0V, 20V

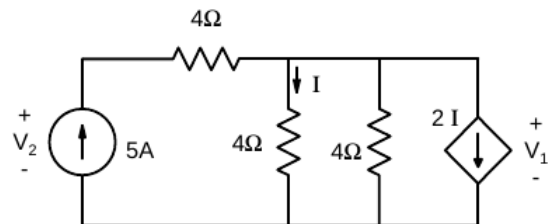


Fig. 101

114) In the figure.102 shown, the switch SW is thrown from position A to position B at time $t=0$. The energy (in μJ) taken from the 3V source to charge the $0.1 \mu F$ capacitor from 0V to 3V is

- a) 0.3 b) 0.45 c) 0.9 d) 3

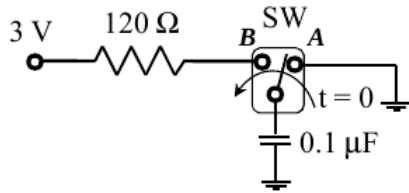


Fig. 102

- a) 44 b) 51 c) 79 d) 108

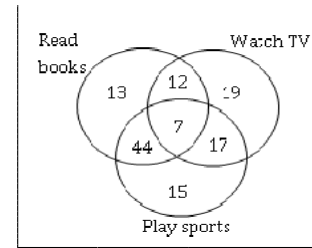


Fig. 105

115) The damping ratio of a series RLC circuit can be expressed as

- a) $\frac{R^2C}{2L}$ c) $\frac{R}{2} \sqrt{\frac{C}{L}}$
 b) $\frac{2L}{R^2C}$ d) $\frac{2}{R} \sqrt{\frac{L}{C}}$

116) In the figure.103 shown, switch SW is closed at $t=0$. Assuming zero initial conditions, the value of $V_c(t)$ (in Volts) at $t=1$ sec is

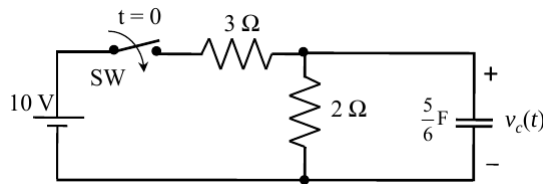


Fig. 103

117) In the given figure.104, the maximum power (in Watts) that can be transferred to the load R_L is

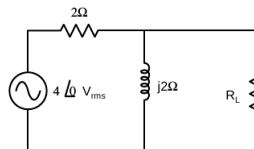


Fig. 104

119) Social science disciplines were in existence in an amorphous form until the colonial period when they were institutionalized. In varying degrees, they were intended to further the colonial interest. In the time of globalization and the economic rise of postcolonial countries like India, conventional ways of knowledge production have become obsolete.

Which of the following can be logically inferred from the above statements?

- (i) Social science disciplines have become obsolete.
- (ii) Social science disciplines had a pre-colonial origin.
- (iii) Social science disciplines always promote colonialism.
- (iv) Social science must maintain disciplinary boundaries.

A (ii)only C (ii) and (iv) only

B (i) and (iii) only D (iii) and (iv) only

118) The Venn diagram.105 shows the preference of the student population for leisure activities. From the data given, the number of students who like to read books or play sports is

120) Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock?

- a) 8:15 b) 11:15 c) 12:15 d) 12:45

121) In the given circuit.106, each resistor has a value equal to 1Ω What is the equivalent resistance across the terminals a and b?

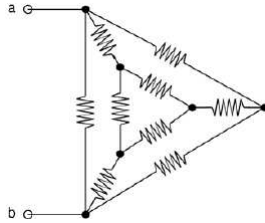


Fig. 106

- a) $\frac{1}{6}\Omega$ b) $\frac{1}{3}\Omega$ c) $\frac{9}{20}\Omega$ d) $\frac{8}{15}\Omega$

122) In the circuit shown in the figure.107, the magnitude of the current (in amperes) through R_2 is

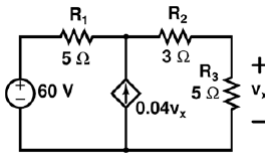


Fig. 107

123) In the circuit.108 shown, V is a sinusoidal voltage source. The current I is in phase with voltage V.

The ratio $\frac{\text{amplitude of voltage across the capacitor}}{\text{amplitude of voltage across the resistor}}$ is

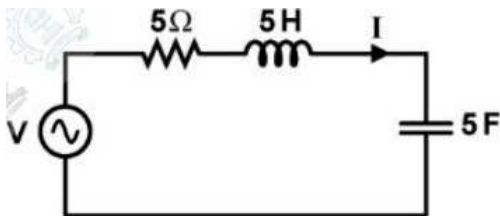


Fig. 108

124) The switch in the circuit.109 shown in the figure was open for a long time and is closed

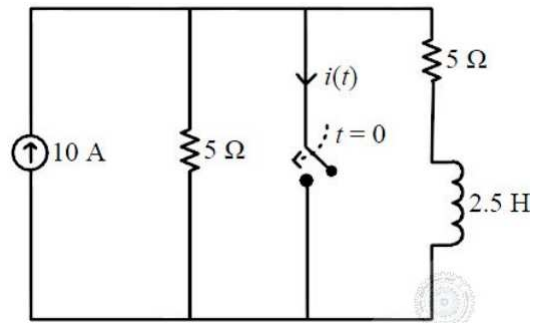


Fig. 109

at $t=0$. The current $i(t)$ (in ampere) at $t=0.5$ seconds

125) Consider the circuit shown in the figure.110. The Thevenin equivalent resistance (in Ω) across P-Q is

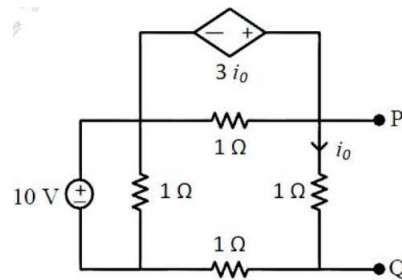


Fig. 110