

# Digital Design through Pi

G V V Sharma\*

## CONTENTS

<b>1</b>	<b>Display Control through Hardware</b>	<b>1</b>
1.1	Components . . . . .	1
1.2	Software Setup . . . . .	1
1.3	Powering the Display . . . . .	1
1.4	Controlling the Display . . . . .	2
<b>2</b>	<b>Display Control through Software</b>	<b>3</b>
2.1	Driving the Segments . . . . .	3
2.2	Counting Decoder . . . . .	4
2.3	Display Decoder . . . . .	5
<b>3</b>	<b>Decade Counter through Flip-Flops</b>	<b>5</b>
	<b>References</b>	<b>5</b>

Component	Value	Quantity
Breadboard		1
Resistor	$\geq 220\Omega$	1
Pi	Model B, Rev 3	1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
Jumper Wires	Female-Male	20

TABLE 1.1

*Abstract*—This manual covers the entire breadth of digital design by building a decade counter using a Raspberry Pi. In the process, boolean logic, combinational logic and sequential logic are covered.

```
git clone git://git.drogon.net/wiringPi
cd ~/wiringPi
./build
```

## 1 DISPLAY CONTROL THROUGH HARDWARE

### 1.1 Components

The components required for this manual are listed in Table 1.1

### 1.2 Software Setup

The following commands will install the Wiring Pi module [2]

```
sudo apt-get install git-core
sudo apt-get update
sudo apt-get upgrade
cd
```

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadevall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

### 1.3 Powering the Display

The breadboard can be divided into 5 segments. In each of the green segments, the pins are internally connected so as to have the same voltage. Similarly, in the central segments, the pins in each column are internally connected in the same fashion as the blue columns.

**Problem 1.1.** Plug the display to the breadboard in Fig. 1.1

The seven segment display in Fig. 1.2 has eight pins, *a, b, c, d, e, f, g* and *dot* that take an active LOW input, i.e. the LED will glow only if the input is connected to ground. Each of these pins is connected to an LED segment. The *dot* pin is reserved for the  $\cdot$  LED.

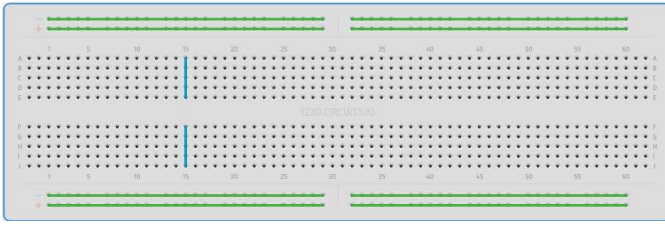


Fig. 1.1

**Problem 1.2.** Connect one end of the resistor to the COM pin of the display and the other end to an extreme pin of the breadboard.

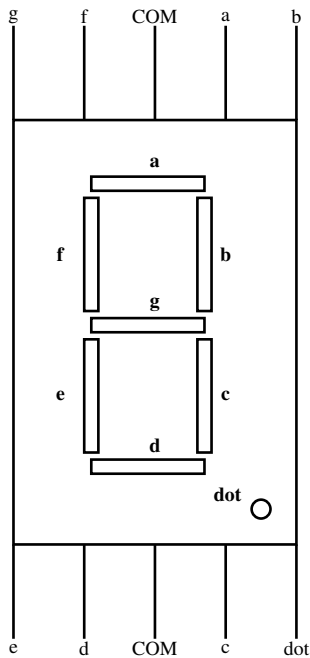


Fig. 1.2

The Raspberry Pi 3 has 40 pins (see Figs. 2.1.1 and 2.1.2), which include power pins that can generate 5V and 3.3V, GND pins, PWM pins, pins for wired communication and some free pins for digital I/O. In the following exercises, only the GND, 5V and digital I/O pins will be used.

**Problem 1.3.** Connect pin 2 (5V) of the Pi to an extreme pin that is in the same segment as the resistor pin.

**Problem 1.4.** Connect pin 6 (GND) of the Pi to the opposite extreme pin of the breadboard

**Problem 1.5.** Connect the *dot* pin of the display to a pin in the same segment as the GND pin. What

do you observe?

#### 1.4 Controlling the Display

Fig. 1.6 explains how to get decimal digits using the seven segment display.

**Problem 1.6.** Generate the number 1 on the display by connecting only the pins *b* and *c* to GND.

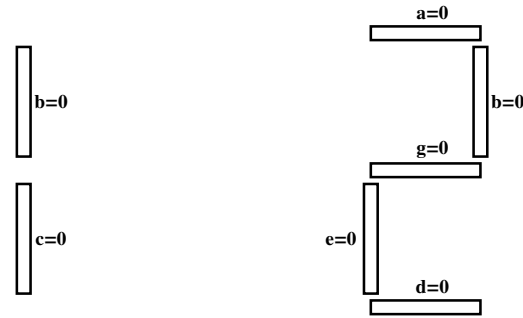


Fig. 1.6

**Problem 1.7.** Repeat the above exercise to generate the number 2 on the display.

**Problem 1.8.** Table 1.8 summarizes the process of generating the decimal digits. 0 means connecting to ground and 1 means not connecting. Complete Table 1.8 for all numbers between 0-9.

a	b	c	d	e	f	g	decimal
1	0	0	1	1	1	1	1
0	0	1	0	0	1	0	2

TABLE 1.8

**Problem 1.9.** Now generate all numbers between 0-9 on the display using the above table.

The 7447 IC helps in displaying decimal numbers on the seven segment display. The  $\bar{a} - \bar{g}$ , pins of the 7447 IC are connected to the *a - g* pins of the display.  $V_{cc}$  should be connected to a 5V power source. The input pins of the decoder are A,B,C and D, with A being the lowest significant bit (LSB) and D being the most significant bit (MSB). For example, the number 5 is visible on the display when the A,B,C and D inputs are the following.

D	C	B	A	Decimal
0	1	0	1	5

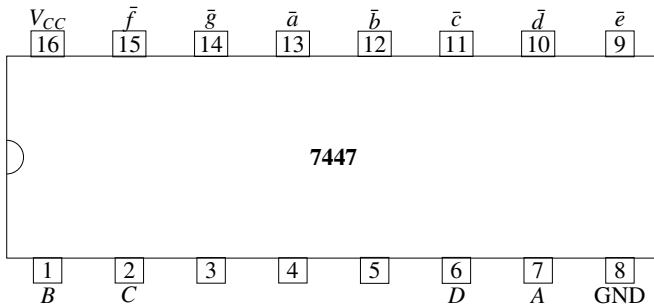


Fig. 1.9

**Problem 1.10.** Connect the 7447 IC decoder  $\bar{a} - \bar{g}$  pins to the  $a - g$  pins of the display respectively.

**Problem 1.11.** Connect the  $V_{cc}$  and GND pins of the decoder to the 5V supply and GND pins of the breadboard.

**Problem 1.12.** Connect the A,B,C,D pins to pins in the GND extreme segment of the breadboard. What do you observe.

**Problem 1.13.** Now remove the D pin from the breadboard and observe the display output.

**Problem 1.14.** Generate a table with A,B,C,D inputs and the equivalent decimal number output.

## 2 DISPLAY CONTROL THROUGH SOFTWARE

### 2.1 Driving the Segments

**Problem 2.1.** Connect the A-D pins of the 7447 IC in Fig. 1.9 to the GPIO pins 0-3 of the Pi shown in Figs. 2.1.1 and 2.1.2.



Fig. 2.1.1: GPIO pin snapshot on Pi [1].

**Problem 2.2.** Type the following code and execute. What do you observe?

```
#include <wiringPi.h>
int main (void)
{
    wiringPiSetup () ;
```

Raspberry Pi 3 Model B (J8 Header)					
GPIO#	NAME		NAME	GPIO#	
	3.3 VDC Power	1		2	5.0 VDC Power
8	GPIO 8 SDA1 (I2C)	3		4	5.0 VDC Power
9	GPIO 9 SCL1 (I2C)	5		6	Ground
7	GPIO 7 GPCLK0	7		8	GPIO 15 TxD (UART) 15
	Ground	9		10	GPIO 16 RxD (UART) 16
0	GPIO 0	11		12	GPIO 1 PCM_CLK/PWM0 1
2	GPIO 2	13		14	Ground
3	GPIO 3	15		16	GPIO 4 4
	3.3 VDC Power	17		18	GPIO 5 5
12	GPIO 12 MOSI (SPI)	19		20	Ground
13	GPIO 13 MISO (SPI)	21		22	GPIO 6 6
14	GPIO 14 SCLK (SPI)	23		24	GPIO 10 CE0 (SPI) 10
	Ground	25		26	GPIO 11 CE1 (SPI) 11
30	SDA0 (I2C ID EEPROM)	27		28	SCL0 (I2C ID EEPROM) 31
21	GPIO 21 GPCLK1	29		30	Ground
22	GPIO 22 GPCLK2	31		32	GPIO 26 PWM0 26
23	GPIO 23 PWM1	33		34	Ground
24	GPIO 24 PCM_FS/PWM1	35		36	GPIO 27 27
25	GPIO 25	37		38	GPIO 28 PCM_DIN 28
	Ground	39		40	GPIO 29 PCM_DOUT 29

**Attention!** The GPIO pin numbering used in this diagram is intended for use with WiringPi / Pi4J. This pin numbering is not the raw Broadcom GPIO pin numbers.

<http://www.pi4j.com>

Fig. 2.1.2: GPIO Wiring Pi [2] pin configuration.

```
pinMode (0, OUTPUT) ;
pinMode (1, OUTPUT) ;
pinMode (2, OUTPUT) ;
pinMode (3, OUTPUT) ;
for (;;)
{
    digitalWrite (0, 1);
    digitalWrite (1, 0) ;
    digitalWrite (2, 1) ;
    digitalWrite (3, 0) ;
}
return 0 ;
```

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE 2.4

```
//Command for raspberry pi
//Save file as bcd_seven.c
//gcc -Wall -o test bcd_seven.c -
//lwiringPi
//followed by
//sudo ./test
```

**Problem 2.3.** Now generate the numbers 0-9 by modifying the above program.

## 2.2 Counting Decoder

In the truth table in Table 2.4,  $W, X, Y, Z$  are the inputs and  $A, B, C, D$  are the outputs. This table represents the system that increments the numbers 0-8 by 1 and resets the number 9 to 0. Note that  $D = 1$  for the inputs 0111 and 1000. Using *boolean* logic,

$$D = WXYZ' + W'X'YZ \quad (2.3.1)$$

Note that 0111 results in the expression  $WXYZ'$  and 1000 yields  $W'X'YZ$ .

**Problem 2.4.** Write the boolean logic functions for  $A, B, C$  in terms of  $W, X, Y, Z$ .

**Problem 2.5.** Write a program for implementing Table 2.4.

**Solution:**

```
#include <wiringPi.h>
int main (void)
{
    int Z=0,Y=0,X=1,W=1;
    int D,C,B,A;
```

```
wiringPiSetup () ;
pinMode (0, OUTPUT) ;
pinMode (1, OUTPUT) ;
pinMode (2, OUTPUT) ;
pinMode (3, OUTPUT) ;
for (;;)
{
    D = (W&&X&&Y&&!Z) || (!W&&!X&&!Y
        &&Z);
    C = (W&&X&&!Y&&!Z) || (!W&&!X&&Y
        &&!Z) || (W&&!X&&Y&&!Z) || (!W
        &&X&&Y&&!Z);
    B = (W&&!X&&!Y&&!Z) || (!W&&X&&!
        Y&&!Z) || (W&&!X&&Y&&!Z) || (!
        W&&X&&Y&&!Z);
    A = (!W&&!X&&!Y&&!Z) || (!W&&X
        &&!Y&&!Z) || (!W&&!X&&Y&&!Z)
        || (!W&&X&&Y&&!Z) || (!W&&!X
        &&Y&&Z);

    digitalWrite (0, A);
    digitalWrite (1, B) ;
    digitalWrite (2, C) ;
    digitalWrite (3, D) ;
}
return 0 ;
}
```

**Problem 2.6.** Verify if your logic is correct by observing the output on the seven segment display for different inputs.

**Problem 2.7.** Connect GPIO pin 10 to the dot pin of the display and execute the following code.

```
#include <wiringPi.h>
int main (void)
{
    wiringPiSetup () ;
    pinMode (10, OUTPUT) ;
    for (;;)
    {
        digitalWrite (10, HIGH) ;
        delay (500) ;
        digitalWrite (10, LOW) ;
        delay (500) ;
    }
}
```

```

return 0 ;
}

```

**Problem 2.8.** A decade counter counts the numbers from 0-9 and then resets to 0. Suitable modify the above programs to obtain a decade counter.

### 2.3 Display Decoder

**Problem 2.9.** Now write the truth table for the seven segment display decoder (IC 7447). The inputs will be  $A, B, C, D$  and the outputs will be  $a, b, c, d, e, f, g$ .

**Problem 2.10.** Obtain the logic functions for outputs  $a, b, c, d, e, f, g$  in terms of the inputs  $A, B, C, D$ .

**Problem 2.11.** Disconnect the Pi from IC 7447 and connect the pins GPIO 0-6 in the Pi directly to the seven segment display.

**Problem 2.12.** Write a new program to implement the logic in Problem 2.10 and observe the output in the display. You have designed the logic for IC 7447!

**Problem 2.13.** Now include your counting decoder program in the display decoder program and see if the display shows the consecutive number.

### 3 DECADE COUNTER THROUGH FLIP-FLOPS

The 7474 IC in Fig. 3.0 has two D flip flops. The D pins denote the input and the Q pins denote the output. CLK denotes the clock input.

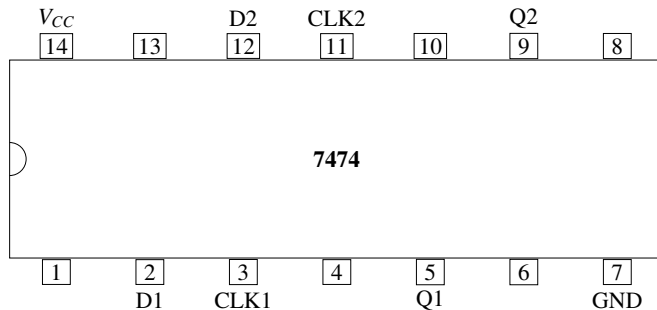


Fig. 3.0

**Problem 3.1.** Connect the 0-3 pins of the Pi to the Q pins of the two 7474 ICs. Use the 0-3 pins as Pi input.

**Problem 3.2.** Connect the Q pins to IC 7447 Decoder as input pins. Connect the 7447 IC to the seven segment display.

**Problem 3.3.** Connect the 11-14 pins of the Pi to the D input pins of two 7474 ICs. Use the 11-14 pins as Pi output.

**Problem 3.4.** Connect pin 10 of the Pi to the CLK inputs of both the 7474 ICs.

**Problem 3.5.** Connect pins 1,4,10 and 13 of both the 7474 ICs to 5V.

**Problem 3.6.** Using the logic for the counting decoder in the Pi software, implement the decade counter.

### REFERENCES

- [1] [Online]. Available: <http://pi4j.com/pins/model-2b-rev1.html>
- [2] [Online]. Available: <http://wiringpi.com/>