

Digital Clock through Arduino

G V V Sharma*

CONTENTS

1	Components	1
2	Hardware Connections	1
3	Display Control through Arduino Software	2

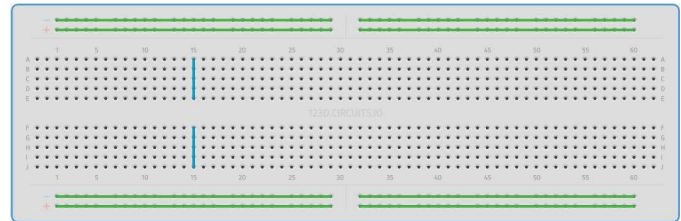


Fig. 2.1

1 COMPONENTS

Component	Value	Quantity
Breadboard		1
Resistor	$\geq 220\Omega$	2
Arduino	Uno	1
Seven Segment Display	Common Anode	2
Jumper Wires		20

TABLE 1.0

2 HARDWARE CONNECTIONS

The breadboard can be divided into 5 segments. In each of the green segments, the pins are internally connected so as to have the same voltage. Similarly, in the central segments, the pins in each column are internally connected in the same fashion as the blue columns.

Problem 2.1. Plug the display to the breadboard in Fig. 2.1

The seven segment display in Fig. 2.2 has eight pins, *a, b, c, d, e, f, g* and *dot* that take an active LOW input, i.e. the LED will glow only if the input is connected to ground. Each of these pins

is connected to an LED segment. The *dot* pin is reserved for the \cdot LED.

Problem 2.2. Connect one end of the resistor to the COM pin of the display and the other end to an extreme pin of the breadboard.

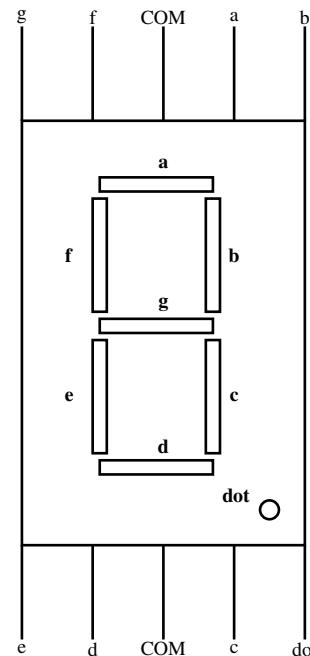


Fig. 2.2

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in.

The Arduino Uno has some ground pins, analog input pins A0-A3 and digital pins D1-D13 that can

be used for both input as well as output. It also has two power pins that can generate 3.3V and 5V. In the following exercises, only the GND, 5V and digital pins will be used.

Problem 2.3. Connect the 5V pin of the arduino to an extreme pin that is in the same segment as the 1K resistor pin.

Problem 2.4. Connect the GND pin of the arduino to the opposite extreme pin of the breadboard

Problem 2.5. Connect the D2-D8 pins of the arduino to the a-g pins of the seven segment display.

Problem 2.6. Connect the D9 pin of the arduino to the free COM pin of the seven segment display.

Problem 2.7. Connect the Arduino to the computer.

3 DISPLAY CONTROL THROUGH ARDUINO SOFTWARE

Problem 3.1. Execute the following code. What do you observe?

```
// Declarations
int A=0,B=0,C=0,D=0,a,b,c,d,e,f,g,
    W,X,Y,Z,i,j,thisPin;
int ledPins
    []={2,3,4,5,6,7,8,9,10};
int pinCount=9;
int r0;
unsigned int initialtime, elapsed;
void showit(int x);

void setup()
{
    //Declaring output pins
    for( thisPin=0;thisPin < pinCount;
        thisPin++)
    {
        pinMode(ledPins[thisPin], OUTPUT);
    }
}

void loop()
{
    //Decade Counting
    for( r0=0;r0 <=9;r0++)
    {
        initialtime=millis();
        //Counting 1000 milliseconds
        for(elapsed=0;elapsed <=1000;
            elapsed=millis()-initialtime)
```

```
{
    //Keep display on
    digitalWrite(9,HIGH);

    //Write number to display
    showit(r0);

} //end counting 10 sec
} //end counting 1 sec
} // end void

//Display logic
void showit(int x)
{
    int D,C,B,A;

    //Decimal to Binary conversion
    A=x%2;
    x=x/2;
    B=x%2;
    x=x/2;
    C=x%2;
    x=x/2;
    D=x%2;

    //BCD to seven segment decoder
    a=(!D&&!C&&!B&&A) || (!D&&C&&!B&&A)
        ;
    b=(!D&&C&&!B&&A) || (!D&&C&&B&&!A) ;
    c=(!D&&!C&&B&&!A) ;
    d=(!D&&!C&&!B&&A) || (!D&&C&&!B&&A)
        || (!D&&C&&B&&A) ;
    e=(!D&&!C&&!B&&A) || (!D&&!C&&B&&A)
        || (!D&&C&&!B&&A) || (!D&&C&&B&&A)
        ) || (!D&&C&&B&&A) || (D&&!C&&!B&&A)
        ;
    f=(!D&&!C&&!B&&A) || (!D&&!C&&B&&A)
        || (!D&&!C&&B&&A) || (!D&&C&&B&&A) ;
    g=(!D&&!C&&!B&&A) || (!D&&!C&&!B&&A)
        ) || (!D&&C&&B&&A) ;

    //Writing to display
    digitalWrite(2,a);
    digitalWrite(3,b);
    digitalWrite(4,c);
    digitalWrite(5,d);
    digitalWrite(6,e);
    digitalWrite(7,f);
    digitalWrite(8,g);
}
```

Problem 3.2. Connect one more display to the breadboard and complete the hardware setup. A parallel connection from the D2-D8 pins should be made to the *a – g* pins of this display.

Problem 3.3. Connect the D10 pin of the arduino to the free COM pin of the second display and execute the following code. What do you observe?

```
// Declaration
int A=0,B=0,C=0,D=0,a,b,c,d,e,f,g,
  W,X,Y,Z,i,j,thisPin;
int ledPins
  []={2,3,4,5,6,7,8,9,10};
int pinCount=9,r0,r1;
int low_pins[]={9,10};
int cnt[2];
unsigned int initialtime, elapsed
  =0;
void showit(int x);

// the setup function runs once
// when you press reset or power
// the board

void setup()
{
// initialize digital pin 2 to 10
// as an output
for( thisPin=0;thisPin < pinCount;
  thisPin++)
{
pinMode(ledPins[thisPin], OUTPUT);
}
}
// the loop function runs over and
// over again forever.
void loop()
{
// count 0 to 5, every 10 seconds
for(r1=0;r1 <=5;r1++)
{
//count 0 to 9 with 1 second
// interval
for(r0=0;r0 <=9;r0++)
{
// number of milliseconds since
// the program started.
initialtime=millis();
```

```
elapsed = initialtime;
//ensuring delay of 1 second
while (elapsed - initialtime <=
  1000)
{
elapsed = millis();

cnt[0] = r0;
cnt[1] = r1;

// Multiplexing Displays
for( i=0;i<2;i++)
{
// turn all the LED(s) LOW
for(j=0;j<2;j++)
digitalWrite(
  low_pins[j],LOW)
;

digitalWrite(low_pins[i],HIGH);
// display digits
showit(cnt[i]);
//allow numbers to be displayed on
// LED before switching
delay(2);
} //end of multiplexing displays
} //end of waiting for 1 second
} //end decade count loop
} //end 0-5 count
}

// function for display decoder
void showit(int x){
int D,C,B,A;
// logic for decimal to binary
A=x%2;
x=x/2;
B=x%2;
x=x/2;
C=x%2;
x=x/2;
D=x%2;
a=(!D&&!C&&!B&&A) || (!D&&C&&!B&&A)
;
b=(!D&&C&&!B&&A) || (!D&&C&&B&&A);
c=(!D&&!C&&B&&A);
d=(!D&&!C&&!B&&A) || (!D&&C&&!B&&A)
|| (!D&&C&&B&&A);
e=(!D&&!C&&!B&&A) || (!D&&!C&&B&&A)
```

```

    || (!D&&C&&B&&A) || (!D&&C&&B&&A
) || (!D&&C&&B&&A) || (D&&C&&B&&A)
;
f = (!D&&C&&B&&A) || (!D&&C&&B&&A)
|| (!D&&C&&B&&A) || (!D&&C&&B&&A);
g = (!D&&C&&B&&A) || (!D&&C&&B&&A
) || (!D&&C&&B&&A);
digitalWrite (2 , a);
digitalWrite (3 , b);
digitalWrite (4 , c);
digitalWrite (5 , d);
digitalWrite (6 , e);
digitalWrite (7 , f);
digitalWrite (8 , g);
}

```

Problem 3.4. Connect 4 more displays and build a 24 hour digital clock.