

# Circuit Analysis

G V V Sharma\*

## CONTENTS

<b>1</b>	<b>Filter</b>	<b>1</b>
1.1	Node Analysis . . . . .	1
1.2	Circuit Analysis . . . . .	3

**Abstract**—This manual provides a quick introduction to Fourier series and Low Pass Filters (LPF), besides facilitating the use of Python for Signals & Systems.

## 1 FILTER

### 1.1 Node Analysis

**Problem 1.1.** Refer to the circuit in Fig. 1.1. Suppose you are told that  $C$  has a resistance given by  $\frac{1}{sC}$ . Find the ratio  $H(s)$  of the output voltage and input voltage using node analysis. The above circuit is known as a low pass filter and  $H(s)$  is known as the transfer function.

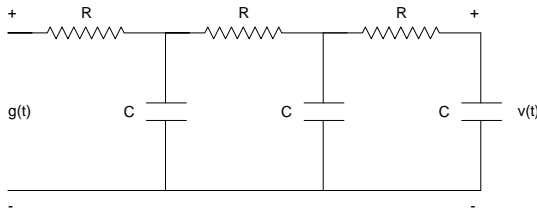


Fig. 1.1: Three stage  $R - C$  low pass filter circuit

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. This work was funded by the PMMMNMTT, MHRD, Govt. of India. All content in this manuscript is released under GNU GPL. Free to use for all.

**Solution:** The equations at the nodes are given by

$$\frac{V_1 - V_i}{R} + sCV_1 + \frac{V_1 - V_2}{R} = 0 \quad (1.1)$$

$$\frac{V_2 - V_1}{R} + sCV_2 + \frac{V_2 - V_o}{R} = 0 \quad (1.2)$$

$$\frac{V_o - V_2}{R} + sCV_o = 0 \quad (1.3)$$

which can be expressed as

$$\begin{pmatrix} sC + \frac{2}{R} & -\frac{1}{R} & 0 \\ -\frac{1}{R} & sC + \frac{2}{R} & -\frac{1}{R} \\ 0 & -\frac{1}{R} & sC + \frac{1}{R} \end{pmatrix} \begin{pmatrix} \frac{V_1}{V_i} \\ \frac{V_2}{V_i} \\ \frac{V_o}{V_i} \end{pmatrix} = \begin{pmatrix} \frac{1}{R} \\ 0 \\ 0 \end{pmatrix} \quad (1.4)$$

Thus,

$$H(s) = \frac{V_o}{V_i} = \frac{\begin{vmatrix} sC + \frac{2}{R} & -\frac{1}{R} & \frac{1}{R} \\ -\frac{1}{R} & sC + \frac{2}{R} & 0 \\ 0 & -\frac{1}{R} & 0 \end{vmatrix}}{\begin{vmatrix} sC + \frac{2}{R} & -\frac{1}{R} & 0 \\ -\frac{1}{R} & sC + \frac{2}{R} & -\frac{1}{R} \\ 0 & -\frac{1}{R} & sC + \frac{1}{R} \end{vmatrix}} \quad (1.5)$$

$$= \frac{1/R^3}{(sC + \frac{1}{R}) \left\{ (sC + \frac{2}{R})^2 - \frac{1}{R^2} \right\} - \frac{1}{R^2} (sC + \frac{2}{R})} \quad (1.6)$$

which can be expressed as

$$H(s) = \frac{1}{(sCR + 1) \left\{ (sCR + 2)^2 - 1 \right\} - (sCR + 2)} \quad (1.7)$$

$$= \frac{1}{(sCR + 2)^3 - (sCR + 2)^2 - 2(sCR + 2) + 1} \quad (1.8)$$

$$= \frac{1}{(sCR)^3 - 5(sCR)^2 + 6sCR + 1} \quad (1.9)$$

**Problem 1.2.** Substitute  $s = j2\pi f, j = \sqrt{-1}$  in (1.9) to obtain  $H(f)$ .  $H(f)$  is known as the frequency response. Plot  $|H(f)|$  in python for  $-20 < f < 20$ ,

given that  $R = 1\text{ k}\Omega$  and  $C = 10\text{ }\mu\text{F}$ .

**Solution:** Type the following code to get Fig. 1.2. You will find that  $H(f)$  is a low pass filter.

```
import numpy as np
import matplotlib.pyplot as plt

#Filter Characteristics

R = 1e3; #10K ohm resistance
C = 10e-6;#10 uF capacitance

#Plotting the filter amplitude
response
T = 0.02;
f_0 = 1/T;
f = np.linspace(-1.5*f_0,1.5*f_0,1
e2)
s = 1j*2*np.pi*f

den = np.polyval([1,-5, 6, 1],s*C*
R);
H = 1/den;

plt.plot(f,abs(H))
plt.grid()# minor
plt.xlabel('$f$ (Hz)')
plt.ylabel('$H(f)$')
#Save figure
plt.savefig('../figs/2.2.eps')
plt.show()
```

**Problem 1.3.** Find the frequency at which  $|H(f)|^2 = \frac{1}{2}$ . This frequency is known as the 3-dB bandwidth of  $H(f)$ .

**Solution:** Substituting  $sCR = jx$  in (1.9),

$$|H(jx)| = \frac{1}{\sqrt{2}} \quad (1.10)$$

$$\Rightarrow -jx^3 + 5x^2 + j6x + 1 = \sqrt{2} \quad (1.11)$$

$$\Rightarrow x^2(6 - x^2)^2 + (1 + 5x^2)^2 = 2 \quad (1.12)$$

$$\Rightarrow x^6 + 13x^4 + 46x^2 - 1 = 0 \quad (1.13)$$

Letting  $y = x^2$ , we obtain the cubic equation

$$y^3 + 13y^2 + 46y - 1 = 0 \quad (1.14)$$

The following script gives the 3 dB bandwidth for

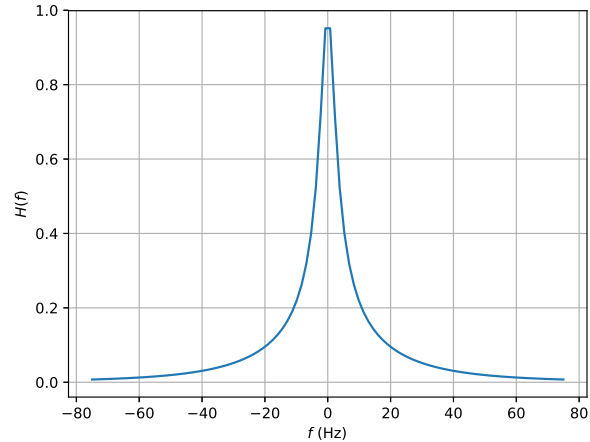


Fig. 1.2: Frequency response of the  $R - C$  filter

the filter  $H$  by choosing the real root.

```
import numpy as np
#Filter Characteristics
R = 1e3; #1K ohm resistance
C = 10e-6;#10 uF capacitance

#finding 3 dB bandwidth
numerically
print(np.sqrt(np.roots([1, 13,
46, -1]))/(2*np.pi*R*C))
```

This yields the value  $f_{3dB} = 2.3395$  Hz.

**Problem 1.4.** Obtain the 3 dB bandwidth by solving the cubic equation in the previous problem

**Solution:** In the above, let  $y = z - \frac{13}{3}$ . Then the equation becomes

$$\Rightarrow z^3 - (31/3)z - 1015/27 = 0 \quad (1.15)$$

This equation has the theoretical solution evaluated by the following script

```
import numpy as np
#Filter Characteristics

R = 1e3; #1K ohm resistance
C = 10e-6;#10 uF capacitance

#finding 3 dB bandwidth
theoretically
```

```

q = -31/3;
r = -1015/27;

print(np.sqrt((-r/2 + np.sqrt(r
**2/4 +q**3/27))**(1/3) + (-r/2
- np.sqrt(r**2/4 +q**3/27))
**(1/3) - 13/3)/(2*np.pi*R*C))

```

Note that this script gives the same result as the one in the previous problem.

## 1.2 Circuit Analysis

**Problem 1.5.** Obtain the expression for  $H(s)$  using mesh analysis.

**Problem 1.6.** Repeat the above exercise using Thevenin's theorem.

**Problem 1.7.** Repeat the above exercise using Norton's theorem.

**Problem 1.8.** Repeat the above exercise using  $Y-\Delta$  transformation.

**Problem 1.9.** Obtain all the two port network parameters for the circuit in Fig. 1.1.