

G V V Sharma\*

## CONTENTS

1	<b>The Decade Counter</b>	1
2	<b>Incrementing Decoder</b>	1
3	<b>Karnaugh Map</b>	1
3.1	K-Map for <i>A</i> . . . . .	1
3.2	K-Map for <i>B</i> . . . . .	2
3.3	K-Map for <i>C</i> . . . . .	3
3.4	K-Map for <i>D</i> . . . . .	3
4	<b>Don't Care Conditions</b>	3
5	<b>Display Decoder</b>	4
6	<b>Finite State Machine</b>	4

*Abstract*—This manual explains Karnaugh maps (K-map) and state machines by deconstructing a decade counter.

## 1 THE DECADE COUNTER

The block diagram of a decade counter (repeatedly counts up from 0 to 9) is available in Fig. 1. The *incrementing* decoder and *display* decoder are part of *combinational* logic, while the *delay* is part of *sequential* logic.

### 2 INCREMENTING DECODER

The incrementing decoder in Fig. 1 takes the numbers 0, 1, . . . , 9 in binary as inputs and generates the consecutive number as output. The corresponding truth table is available in Fig. I.

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

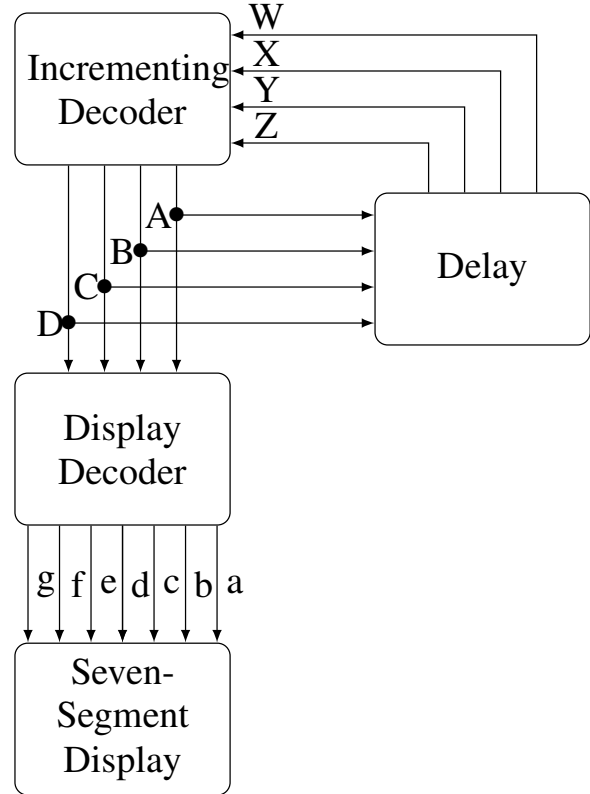


Fig. 1: The decade counter

## 3 KARNAUGH MAP

Using Boolean logic, output *A* in Table I can be expressed in terms of the inputs *W, X, Y, Z* as

$$A = W'X'YZ' + W'XY'Z' + W'X'YZ' + W'XYZ' + WX'Y'Z \quad (1)$$

### 3.1 K-Map for *A*

The expression in (1) can be minimized using the K-map in Fig. 2. In Fig. 2, the *implicants* in boxes 0,2,4,6 result in  $W'Z'$ . The implicants in boxes 0,8

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0

TABLE I

ZY \ XW	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	0	0	0	0
10	1	0	0	0

Fig. 2: K-map for A.

result in  $W'X'Y'$ . Thus, after minimization using Fig. 2, (1) can be expressed as

$$A = W'Z' + W'X'Y' \quad (2)$$

**Problem 1.** Using the fact that

$$X + X' = 1 \quad (3)$$

$$XX' = 0, \quad (4)$$

derive (2) from (1) algebraically.

### 3.2 K-Map for B

From Table I, using boolean logic,

$$B = WX'Y'Z' + W'XY'Z' + WX'YZ' + W'XYZ' \quad (5)$$

ZY \ XW	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	0	0	0
10	0	0	0	0

Fig. 3: K-map for B.

**Problem 2.** Show that (5) can be reduced to

$$B = WX'Z' + W'XZ' \quad (6)$$

using Fig. 3.

**Problem 3.** Derive (6) from (5) algebraically using (3).

ZY \ XW	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	0	0	0	0
10	0	0	0	0

Fig. 4: K-map for C.

### 3.3 K-Map for C

From Table I, using boolean logic,

$$C = WXY'Z' + W'X'YZ' + WX'YZ' + W'XYZ' \quad (7)$$

**Problem 4.** Show that (7) can be reduced to

$$C = WXY'Z' + X'YZ' + W'YZ' \quad (8)$$

using Fig. 4.

**Problem 5.** Derive (8) from (7) algebraically using (3).

		<i>XW</i>			
		00	01	11	10
<i>ZY</i>	00	0	0	0	0
	01	0	0	1	0
	11	0	0	0	0
	10	1	0	0	0

Fig. 5: K-map for D.

### 3.4 K-Map for D

From Table I, using boolean logic,

$$D = WXYZ' + W'X'Y'Z \quad (9)$$

**Problem 6.** Minimize (9) using Fig. 5.

## 4 DON'T CARE CONDITIONS

4 binary digits are used in the incrementing decoder in Fig. 1. However, only the numbers from 0-9 are used as input/output in the decoder and we *don't care* about the numbers from 10-15. This phenomenon can be addressed by revising Table I to obtain Table II.

Z	Y	X	W	D	C	B	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	-	-	-	-
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

TABLE II

		<i>XW</i>			
		00	01	11	10
<i>ZY</i>	00	1	0	0	1
	01	1	0	0	1
	11	-	-	-	-
	10	1	0	-	-

Fig. 6: K-map for A with don't cares.

The revised K-maps for A,B,C,D are now available in Figs. 6-9 resulting in

$$A = W' \quad (10)$$

$$B = WX'Z' + W'X \quad (11)$$

$$C = X'Y + W'Y + WXY' \quad (12)$$

$$D = W'Z + WXY \quad (13)$$

		$XW$			
		00	01	11	10
$ZY$	00	0	1	0	1
	01	0	1	0	1
	11	-	-	-	-
	10	0	0	-	-

Fig. 7: K-map for  $B$  with don't cares.

		$XW$			
		00	01	11	10
$ZY$	00	0	0	0	0
	01	0	0	1	0
	11	-	-	-	-
	10	1	0	-	-

Fig. 9: K-map for  $D$  with don't cares.

		$XW$			
		00	01	11	10
$ZY$	00	0	0	1	0
	01	1	1	0	1
	11	-	-	-	-
	10	0	0	-	-

Fig. 8: K-map for  $C$  with don't cares.

D	C	B	A	a	b	c	d	e	f	g	Decimal
0	0	0	0	1	0	0	1	1	1	1	0
0	0	0	1	0	0	1	0	0	1	0	1
0	0	1	0	0	0	0	0	1	1	0	2
0	0	1	1	1	0	0	1	1	0	0	3
0	1	0	0	0	1	0	0	1	0	0	4
0	1	0	1	0	1	0	0	0	0	0	5
0	1	1	0	0	0	0	1	1	1	1	6
0	1	1	1	1	0	0	0	0	0	0	7
1	0	0	0	0	0	0	1	1	0	0	8
1	0	0	1	0	0	0	0	0	0	1	9

TABLE III: Truth table for display decoder.

which are simpler than (2), (6), (8) and (9).

## 5 DISPLAY DECODER

Table III is the truth table for the display decoder in Fig. 1.

**Problem 7.** Use K-maps to obtain the minimized expressions for  $a, b, c, d, e, f, g$  in terms of  $A, B, C, D$  with and without don't care conditions.

## 6 FINITE STATE MACHINE

Fig. 10 shows a *finite state machine* (FSM) diagram for the decade counter in Fig. 1.  $s_0$  is the state when the input to the incrementing decoder is 0. The *state transition table* for the FSM is Table I where the present state is denoted by the variables  $W, X, Y, Z$  and the next state by  $A, B, C, D$ . The FSM implementation is available in Fig. 11. The *flip-flops* hold the input for the time that is given by the *clock*. This is nothing but the implementation of the *Delay* block in Fig. 1. The hardware cost of the system is given by

$$\text{No. of D Flip-Flops} = \lceil \log_2(\text{No. of States}) \rceil \quad (14)$$

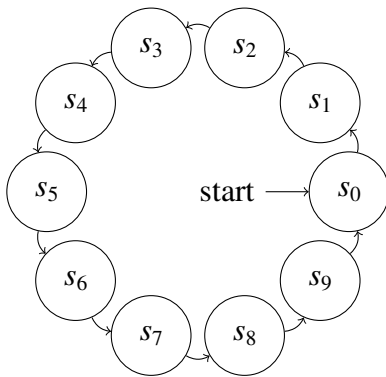


Fig. 10: FSM for the decade counter.

 


Fig. 11: Decade counter FSM implementation using D-Flip Flops.

For the FSM in Fig. 10, the number of states is 9, hence the number flipflops required = 4.

**Problem 8.** Design a decade down counter (counts from 9 to 0 repeatedly) using an FSM.